

Date.....

→ AC Analysis of BJT with active load :-

$$g_{m1} = \frac{I_{C1}}{V_T} = 19.82 \text{ mA/V}, \quad g_{m2} = \frac{I_{C2}}{V_T} = 19.82 \text{ mA/V}, \quad g_{m3} = \frac{I_{C3}}{V_T} = 19.82 \text{ mA/V}, \quad g_{m4} = \frac{I_{C4}}{V_T} = 19.82 \text{ mA/V}$$


$$r_{o1} = \frac{V_A}{I_{C1}} = \frac{100}{512.425 \times 10^{-3}} = 195.15 \text{ k}\Omega, \quad r_{o2} = \frac{V_A}{I_{C2}} = \frac{100}{512.425 \times 10^{-3}} = 195.15 \text{ k}\Omega, \quad r_{o3} = \frac{V_A}{I_{C3}} = \frac{100}{512.425 \times 10^{-3}} = 195.15 \text{ k}\Omega, \quad r_{o4} = \frac{V_A}{I_{C4}} = \frac{100}{512.425 \times 10^{-3}} = 195.15 \text{ k}\Omega$$

$$\therefore r_{o1} = r_{o2} = r_{o3} = r_{o4} = r_o$$

$$\therefore g_{m1} = g_{m2} = g_{m3} = g_{m4} = g_m$$

$$r_x = \frac{\beta}{g_m} = 10.09 \text{ k}\Omega$$
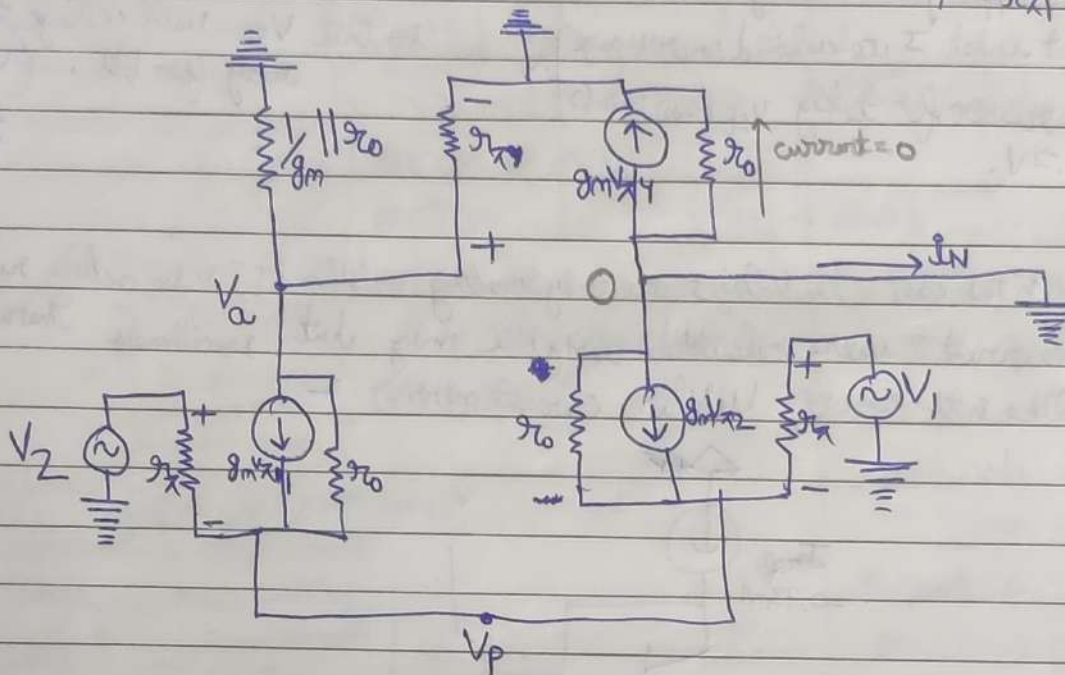
$$\therefore r_{x1} = r_{x2} = r_{x3} = r_{x4}$$



$$\frac{V_2 - V_P}{r_x} + g_m(V_2 - V_P) + \frac{V_a - V_P}{r_o} + g_m(V_1 - V_P) + \frac{(0 - V_P)}{r_o} + \frac{(V_1 - V_P)}{r_x} = 0$$

$$I_N = g_m(V_a - 0) + g_m(V_1 - V_P) + \frac{(0 - V_P)}{r_o}$$

$$g_m(V_2 - V_P) + \frac{V_a - V_P}{r_o} + \frac{V_a - 0}{\left(\frac{1}{g_m} \parallel r_o\right)} + \frac{V_a - 0}{r_x} = 0$$

$$V_a \left[\frac{1}{r_o} + \frac{1}{r_x} + \frac{1}{r_x} \right] = V_P \left[\frac{1}{r_o} + g_m \right] - g_m V_2$$

Spiral

Date.....

$$V_a = V_p \left(\frac{1}{r_o} + g_m \right) - g_m V_2$$

$$\frac{1}{r_o} + \frac{1}{r_e} + \frac{1}{r_x}$$

$$V_a - V_p = \frac{V_p}{r_o} + V_p g_m - g_m V_2 - \frac{V_p}{r_o} - \frac{V_p}{r_e} - \frac{V_p}{r_x} = V_p \left(g_m - \frac{1}{r_x} - \frac{1}{r_e} \right) - g_m V_2$$

$$\frac{1}{r_o} + \frac{1}{r_e} + \frac{1}{r_x} \quad \frac{1}{r_o} + \frac{1}{r_e} + \frac{1}{r_x}$$

$$\frac{V_2}{r_x} + g_m V_2 - \frac{g_m V_2}{1 + \frac{r_o}{r_e} + \frac{r_o}{r_x}} + g_m V_1 + \frac{V_1}{r_x} = \frac{V_p}{r_x} + g_m V_p - V_p \left(g_m - \frac{1}{r_x} - \frac{1}{r_e} \right)$$

$$+ V_p \left(g_m + \frac{1}{r_o} + \frac{1}{r_x} \right)$$

$$RHS = V_p \left(\frac{1}{r_x} + g_m + \frac{\frac{1}{r_x} + \frac{1}{r_e} - g_m}{1 + \frac{r_o}{r_e} + \frac{r_o}{r_x}} + g_m + \frac{1}{r_o} + \frac{1}{r_x} \right)$$

$$= V_p \left(\frac{2}{r_x} + 2g_m + \frac{1}{r_o} + \frac{r_e + r_x - g_m r_x r_e}{r_x r_e} \times \frac{r_e r_x}{r_e r_x + r_o(r_x + \frac{1}{g_m})} \right)$$

$$= V_p \left(\frac{2}{r_x} + 2g_m + \frac{1}{r_o} + \frac{\frac{1}{g_m} + r_x - \frac{1}{g_m}}{\frac{1}{g_m}} \times \frac{r_e}{r_e r_x + r_o(r_x + \frac{1}{g_m})} \right)$$

$$= V_p \left(\frac{2}{r_x} + 2g_m + \frac{1}{r_o} + \frac{1}{r_x + r_o + r_o r_x g_m} \right) = V_p \left(\frac{2}{r_x} + 2g_m + \frac{1}{r_o} + \frac{1}{r_x + r_o + r_o r_x g_m} \right)$$

$$LHS = V_2 g_m + \frac{V_2}{r_x} - \cancel{\frac{g_m V_2}{1 + \frac{r_o}{r_e} + \frac{r_o}{r_x}}} + (g_m + \frac{1}{r_x}) V_1$$

$$LHS = V_2 g_m + \frac{V_2}{r_x} - \frac{g_m V_2}{r_x (1 + r_o g_m) + r_o} = g_m (V_1 + V_2) - \frac{g_m r_x V_2}{r_o (g_m r_x + 1)}$$

Spiral

Date.....

If $V_2 = -V_1$ then $V_p = 0$

$$V_p(42.4) = 19.82V_1 + 19.82V_2 \Rightarrow V_p = 0.467(V_1 + V_2)$$

$$V_a = \frac{g_m}{g_m + \frac{1}{r_{\pi}}} (V_p - V_2) = 0.995 (V_p - V_2) = 0.995 (0.467V_1 - 0.53V_2)$$

$$V_a = 0.464V_1 - 0.53V_2$$

$$i_N = 19.82 \times (0.464V_1 - 0.53V_2) + 19.82 (V_1 - 0.467V_1 - 0.53V_2) - \frac{V_p}{r_o}$$

$$i_N = 19.82 [0.464V_1 - 0.53V_2 + 0.533V_1 - 0.467V_2] - (V_p \times 0.0051)$$

$$i_N = 19.82 [0.997V_1 - 0.997V_2] - 0.0024(V_1 + V_2)$$

$$i_N = 19.76V_1 - 19.76V_2 - 0.0024V_1 - 0.0024V_2$$


$$i_N = 19.76(V_1) - 19.76V_2 = 19.76(V_1 - V_2)$$

$$\frac{i_N}{V_1 - V_2} = 19.76 = G_m = \text{Overall transconductance} \approx 19.82 \approx g_m$$

$$R_o = r_{o2} \parallel r_{o4} = r_o \parallel r_o = \frac{r_o}{2} = 97.57 \text{ K}\Omega$$

Date.....

AC Analysis of stage 1

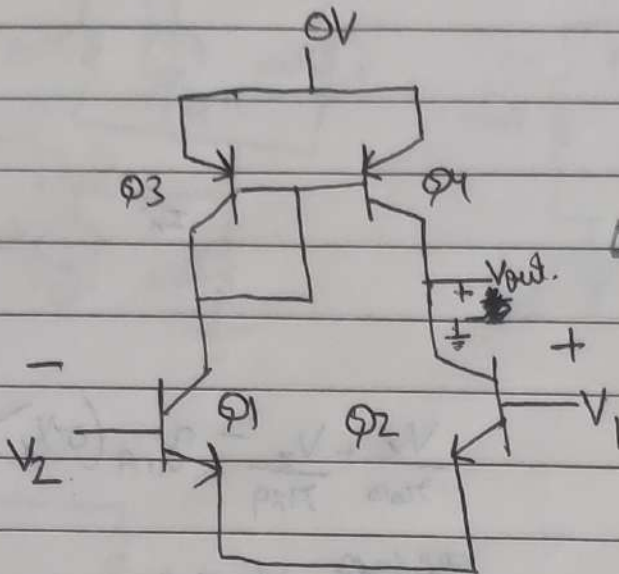

$$\begin{aligned} A_v &= -1933.94 \\ R_{in} &= 20.18 \text{ k}\Omega \\ R_{out} &= 97.57 \text{ k}\Omega \end{aligned}$$

$$A_v = \frac{V_{out}}{v_2 - v_1} = \frac{V_{out}}{-(v_1 - v_2)} = \frac{g_m R_o}{2}$$

$$A_v = \frac{V_{out}}{v_1 - v_2} = -\frac{g_m R_o}{2} = -1933.94$$


Later output resistance is done.

$$R_{in} = R_{id} = 2 \times r_{\pi} = 2 \times 10.09 = 20.18 \text{ k}\Omega$$

differential input resistance

} doubtful, confirm it.

combine all stages
↓


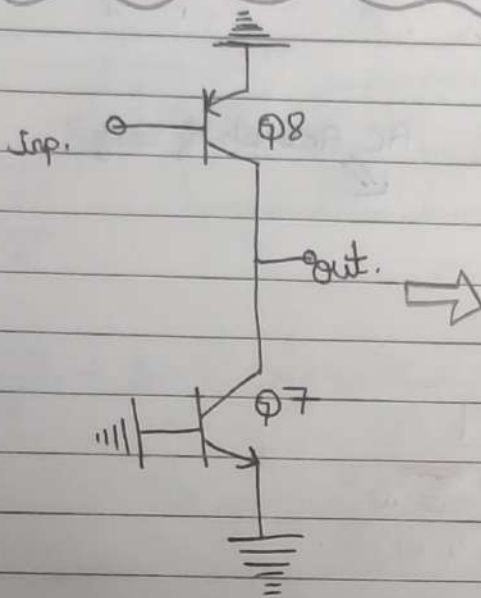


AC analysis of Stage 2

$A_v, R_i, R_o = ?$


$$\begin{aligned} A_v &= -1940.056 \\ R_i &= 6.3 \text{ k}\Omega \\ R_o &= 61.16 \text{ k}\Omega \end{aligned}$$

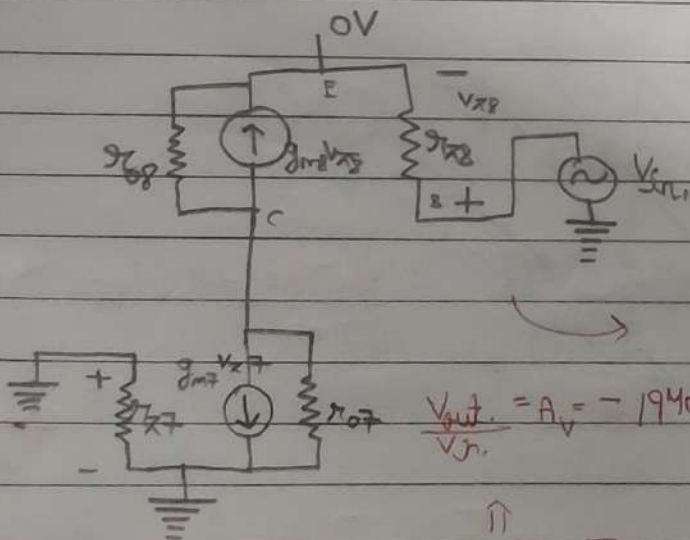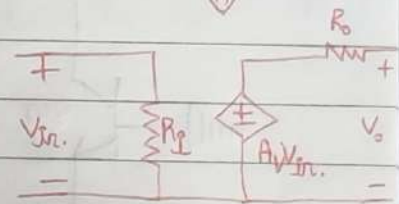* A BJT used as voltage amplifier can be represented as a two port N/W which was studied in Network Theory



$$\frac{V_{out}}{V_{in}} = A_v = -1940.056$$


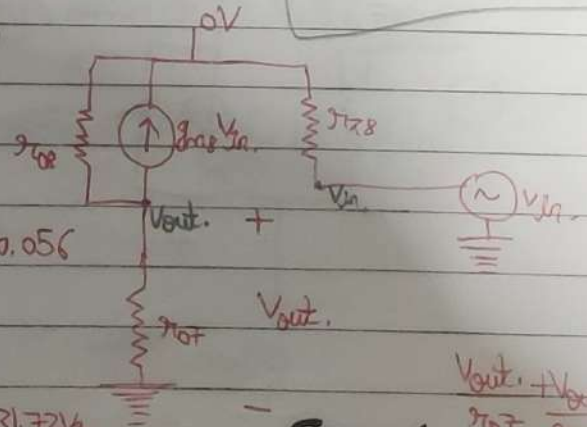
$$V_{out} \left[\frac{1}{122.7} + \frac{1}{121.95} \right] = -31.72 V_{in}$$



$$\frac{V_{out}}{r_{e7}} + \frac{V_{out}}{r_{o8}} = -31.72 V_{in}$$


Spiral

Date.....

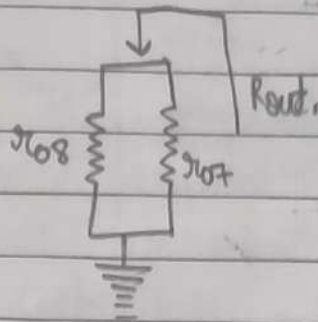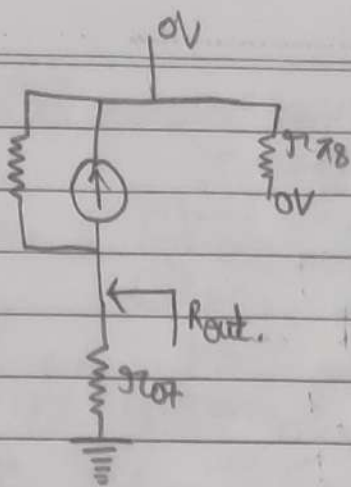

$$\frac{1}{R_{out}} = \frac{1}{2k8} + \frac{1}{2k7}$$
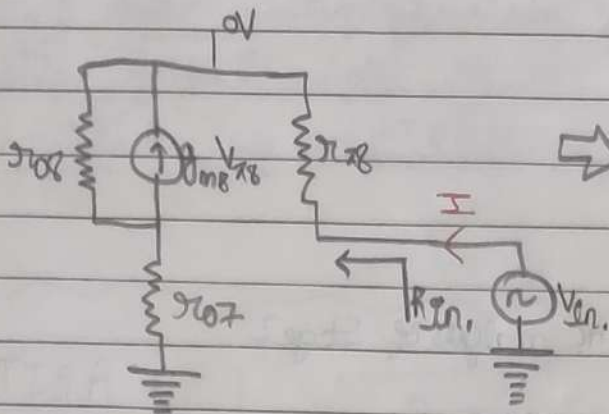
$$R_{out} = \frac{2k8 \cdot 2k7}{2k8 + 2k7} = 61.16 K\Omega$$




$$\frac{V_{tn}}{I_n} = R_{in}$$


$$I \cdot 2k8 = V_{tn}$$

$$\therefore R_{in} = 2k8 = 6.3 K\Omega$$

AC Analysis of Stage 3

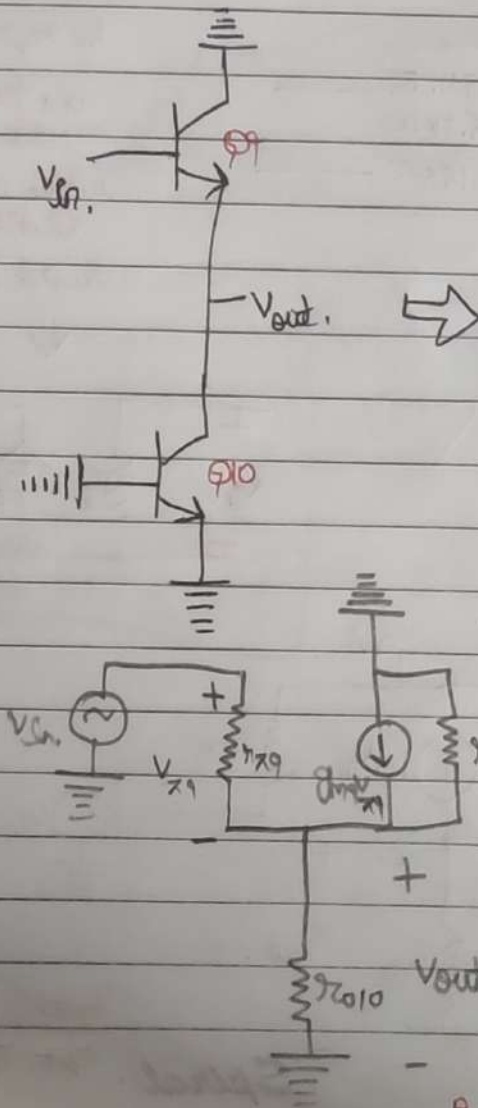
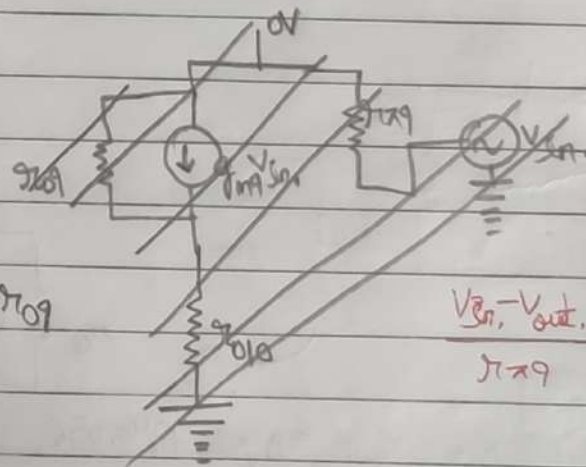
$$\begin{aligned} A_v &= 1 \\ R_{th} &= \frac{R_1 R_2}{R_1 + R_2} = 20.576 \text{ k}\Omega \\ R_o &= 0.031 \text{ k}\Omega \end{aligned}$$




$$\frac{V_{in} - V_{out} + g_m (V_{in} - V_{out}) + \frac{(0 - V_{out})}{r_{o10}}}{r_{\pi 9}} = \frac{V_{out}}{r_{o10}}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{32.58}{32.57} = 0.9997 \approx 1$$

Spiral


Date.....

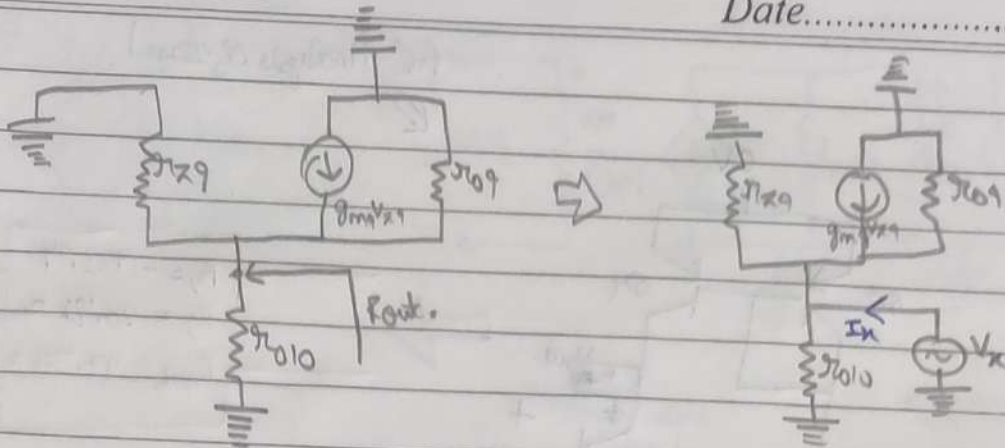

$$\frac{V_x}{r_{010}} + \frac{V_x}{r_{09}} - g_{m9}(0 - V_x) + \frac{V_x}{r_{09}} = I_x$$

$$R_{out} = 0.031 \text{ k}\Omega$$
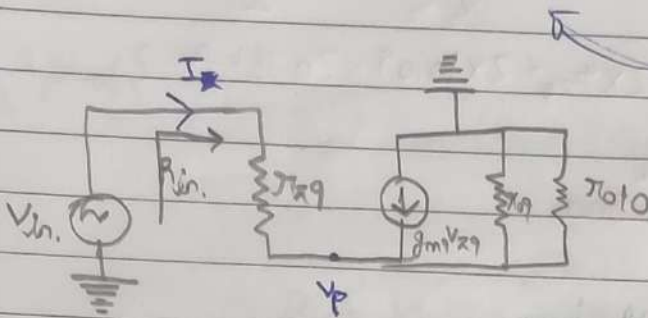
$$\frac{V_x}{I_x} = R_{out} = \frac{1}{\frac{1}{r_{010}} + \frac{1}{r_{09}} + g_{m9} + \frac{1}{r_{09}}}$$



$$\frac{V_{in}}{I} = R_{in}$$

$$R_{eq} = \frac{r_{09} r_{010}}{r_{09} + r_{010}}$$

$$\frac{V_{in} - V_p}{r_{09}} + g_{m9}(V_{in} - V_p) = \frac{V_p}{R_{eq}} = \frac{V_p (r_{09} + r_{010})}{r_{09} r_{010}}$$

$$V_{in} \left[g_{m9} + \frac{1}{r_{09}} \right] = V_p \left[\frac{r_{09} + r_{010}}{r_{09} r_{010}} + g_{m9} + \frac{1}{r_{09}} \right] = V_p \left[\frac{1}{r_{010}} + \frac{1}{r_{09}} + g_{m9} + \frac{1}{r_{09}} \right]$$

$$V_{in} \times 32.58 = V_p \times 32.59$$

$$V_p = V_{in} \times 0.9997 = 0.9997 V_{in}$$



$$\frac{V_{in} - V_p}{r_{09}} = I \Rightarrow I = \frac{0.0003 V_{in}}{6.17} = 4.86 V_{in} \times 10^{-5}$$

$$R_{in} = \frac{V_{in}}{I} = \frac{1}{4.86 \times 10^{-5}} = 20576.13 \text{ k}\Omega$$

P.T.O.

Spiral

Combining all stages
↓

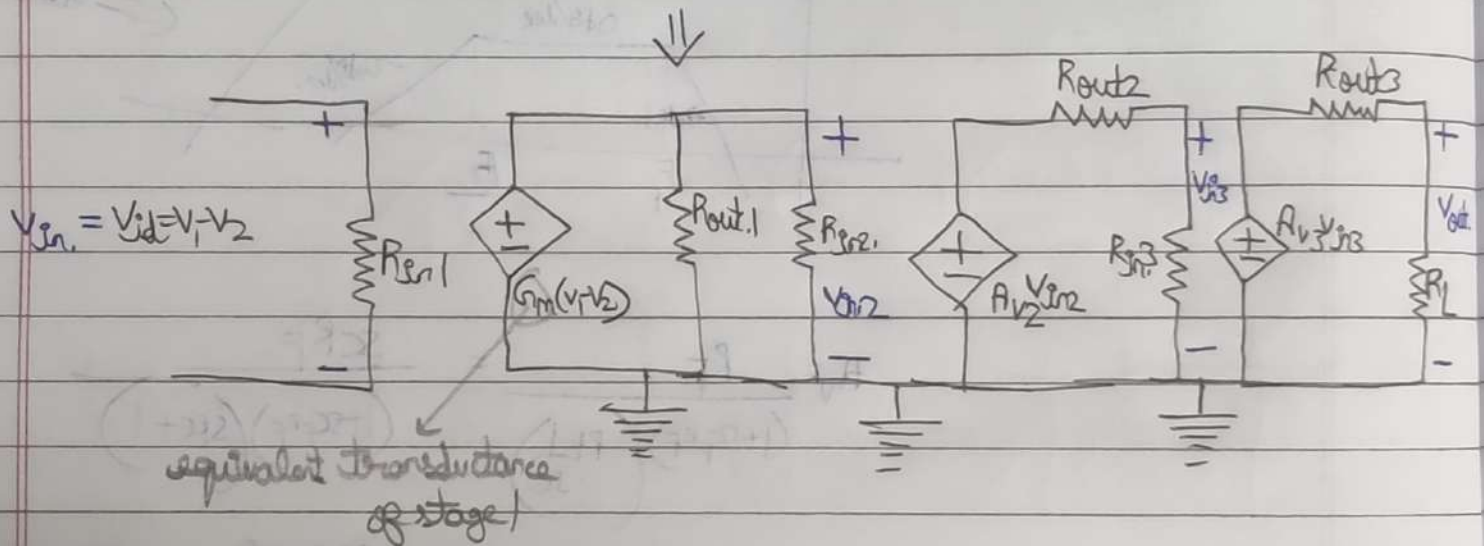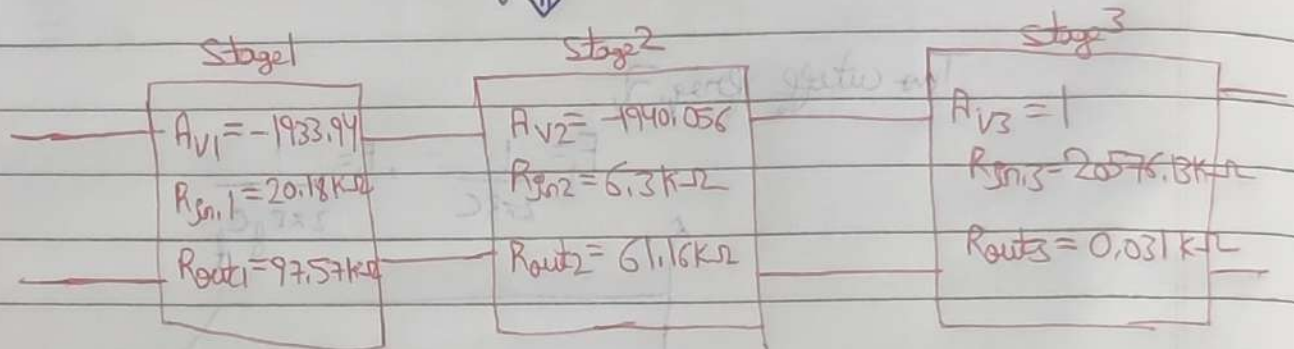

For open loop gain $R_L \rightarrow \infty$ \therefore open circuit on output side

$$A_{OL} = \frac{V_{out}}{V_{in}} = \frac{V_{id2}}{V_{in}} \times \frac{V_{id3}}{V_{id2}} \times \frac{V_{out}}{V_{id3}} = \left[\frac{g_m(V_1 - V_2)}{V_{in}} \times (R_{out1} \parallel R_{in2}) \right] \times \left[\frac{R_{in3}}{R_{out2} + R_{in3}} \right] \times \left[\frac{A_{v2} V_{id2}}{V_{id2}} \right] \times \left[\frac{R_L}{R_L + R_{out3}} \right] \times \left[\frac{A_{v3} V_{id3}}{V_{id3}} \right]$$

$$A_{OL} = 19.82 \times 5.92 \times 1940.056 \times 0.997$$

$$A_{OL} = 226952.4$$

$$A_{OL}(\text{indB}) \approx 108\text{dB}$$